

LECTURE II

Circuit Analysis & Troubleshooting Techniques

SECTION I


Project I Review

Project I Review

- Official Due Date: Friday, November 1st by 11:59PM
- Ask questions and seek help (online or @Lab Hours), so you can finish it on time!
- Note: Your OPS membership is contingent on the completion of Project 1 by the end of Fall Quarter


Learning Concepts:

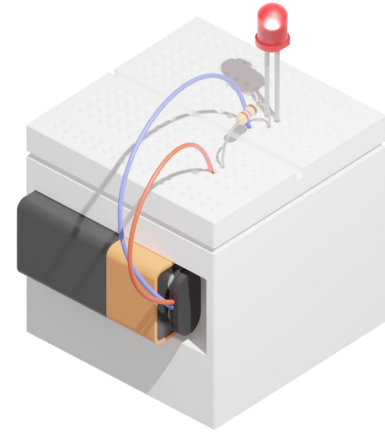- Introduction to Circuits
- Ohm's Law (Voltage, Current, Resistance)
- Breadboarding
- Soldering




Schematic Connections Reminder

Connected Wires

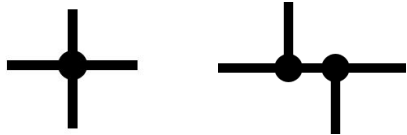

Unconnected Wires



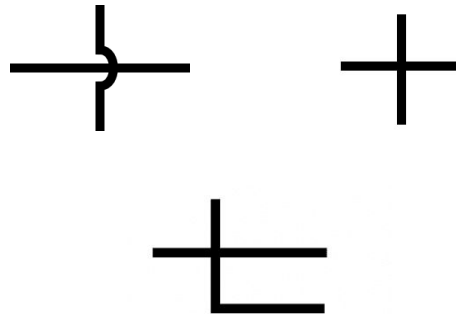


Slide Switch Review

- In project 1, we used the Slide Switch as a Toggle Switch



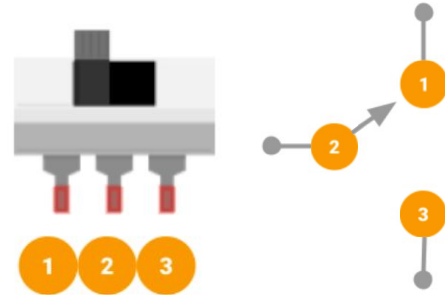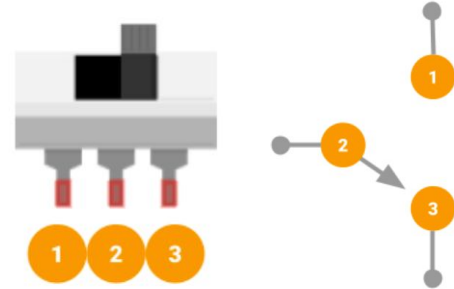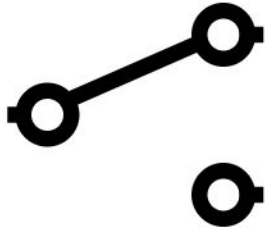- We can also use the slide switch as a Changeover Switch





Breadboarding Quiz!

With the parts given in your OPS Kit, build this circuit on a breadboard.

Tips:

1. Resistor can go before or after the Battery (since you only want 1 LED, 1 Resistor, and 1 Battery in series)
2. A slide switch can be used as a Changeover Switch

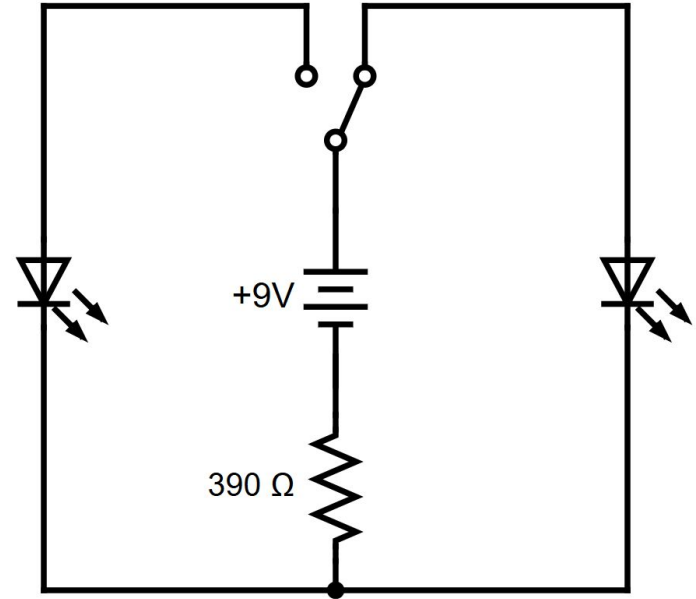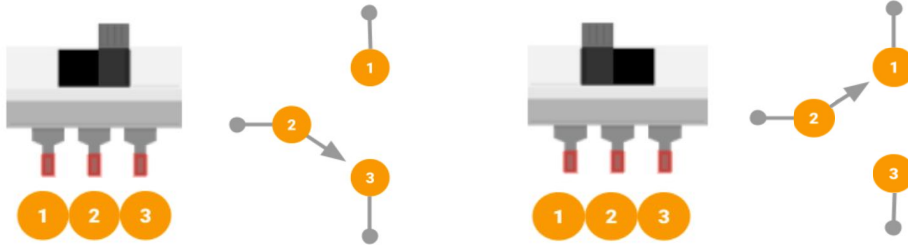

SECTION II


Project II

Project 2 Overview

- Create an **Electronic Piano** with the 555 Timer IC, and solder it to a printed circuit board.


You will learn:

- Circuit Analysis (Nodes, Voltage Drop)
- Circuit Troubleshooting
- Multimeters
- 555 Timer
- Breadboarding
- Soldering


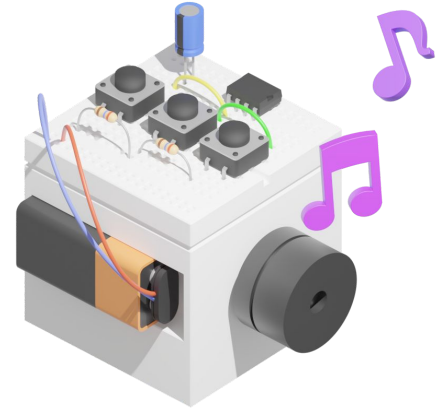


Checkpoint 1

- Create an **Blinking LED Circuit** with the 555 Timer IC
- Part of Project 2 Submission
- Timing of the blinking LED Circuit relies on the capacitor value
 - More on this later!

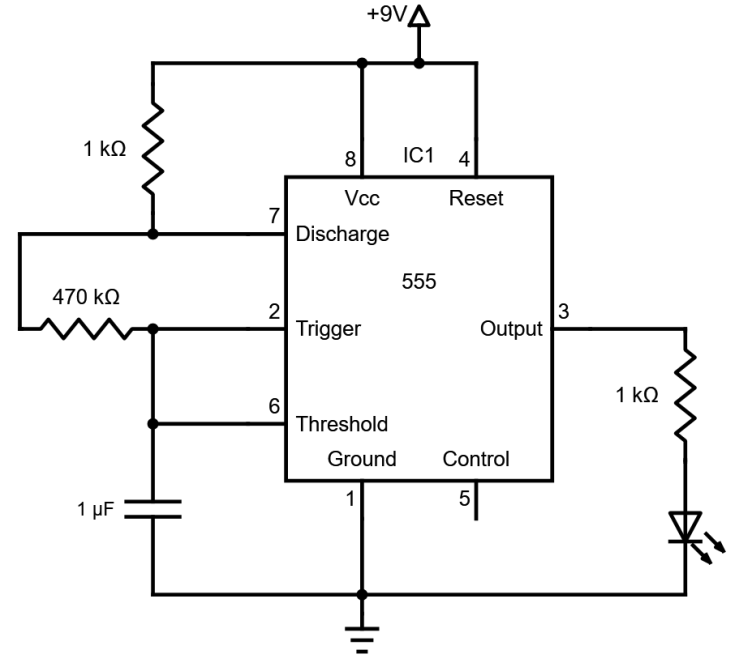

Project 2: 555 Piano

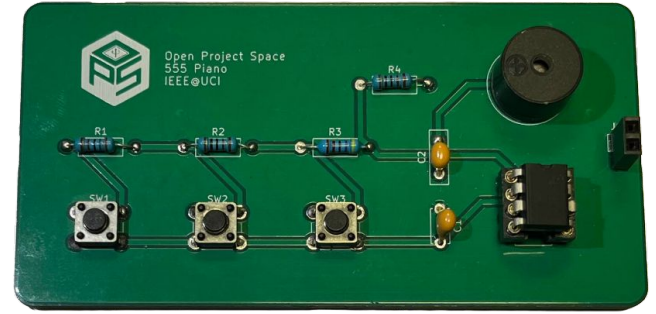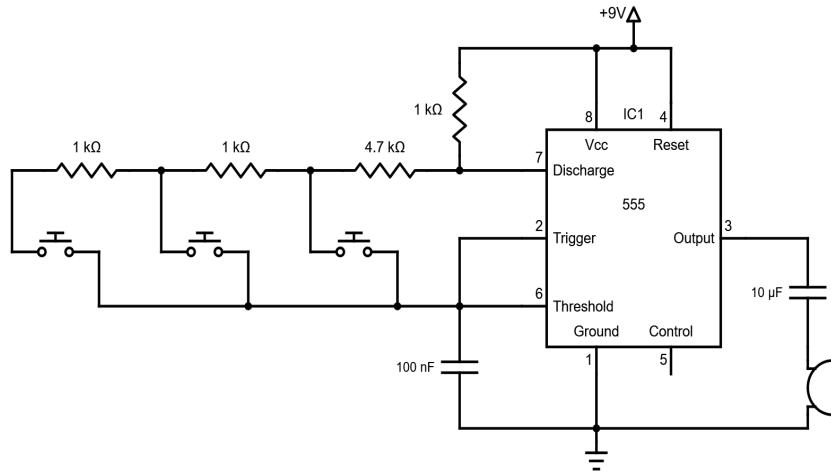


SECTION III

Circuit Topology

Circuits

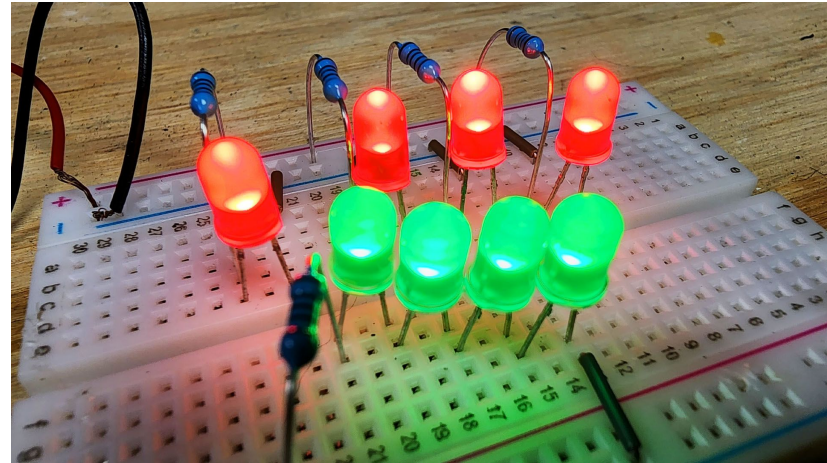
- In project 1, we built a **circuit** with a single **closed loop** path where electrons can flow
- Circuits consist of **nodes** and **loops** to analyze the voltage, current, and resistance across segments of the circuit
 - **Why?** Circuit analysis enables us to design, **debug**, and test the performance of circuits



Nodes


- A **node** is a **connection** between two or more **components**
- All points on the **same node** have the **same voltage**

Node

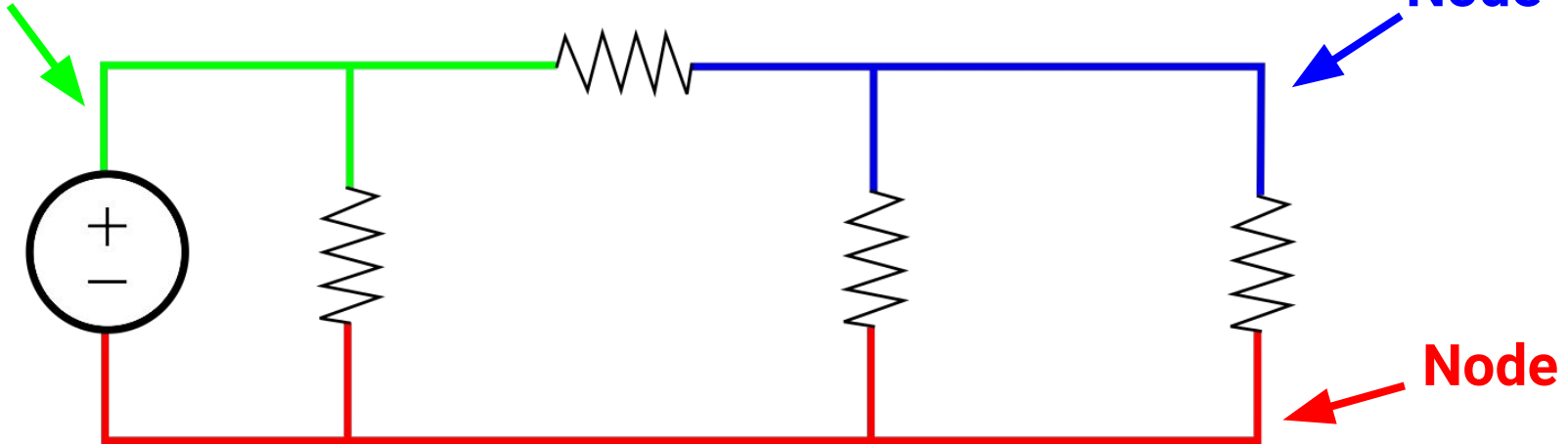

Node Exercise

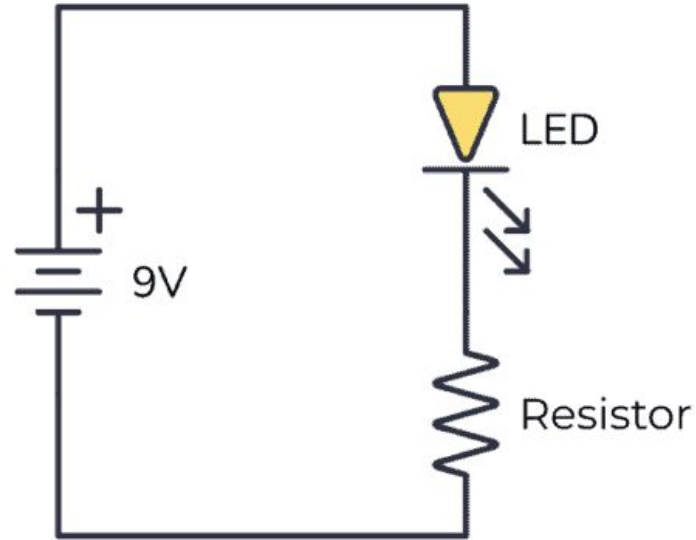
Exercise: How many nodes are in this schematic?



Node Exercise


Exercise: How many nodes are in this schematic?

Answer: 3 Nodes

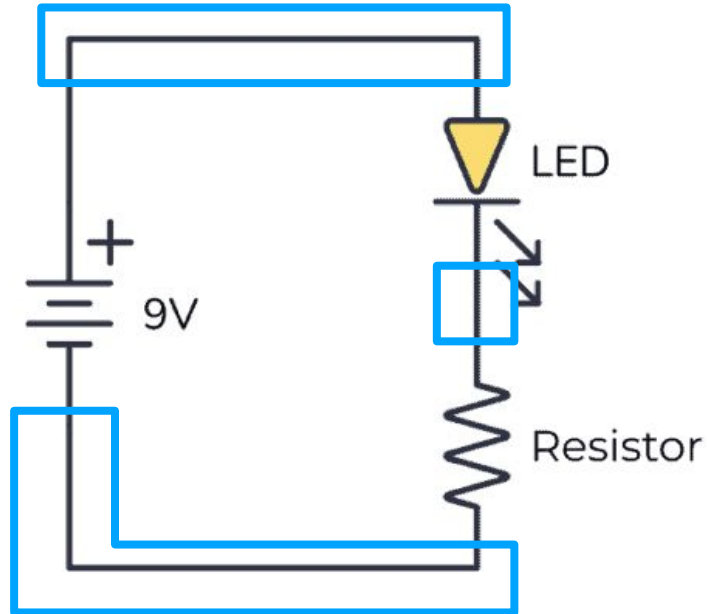

Node Exercise

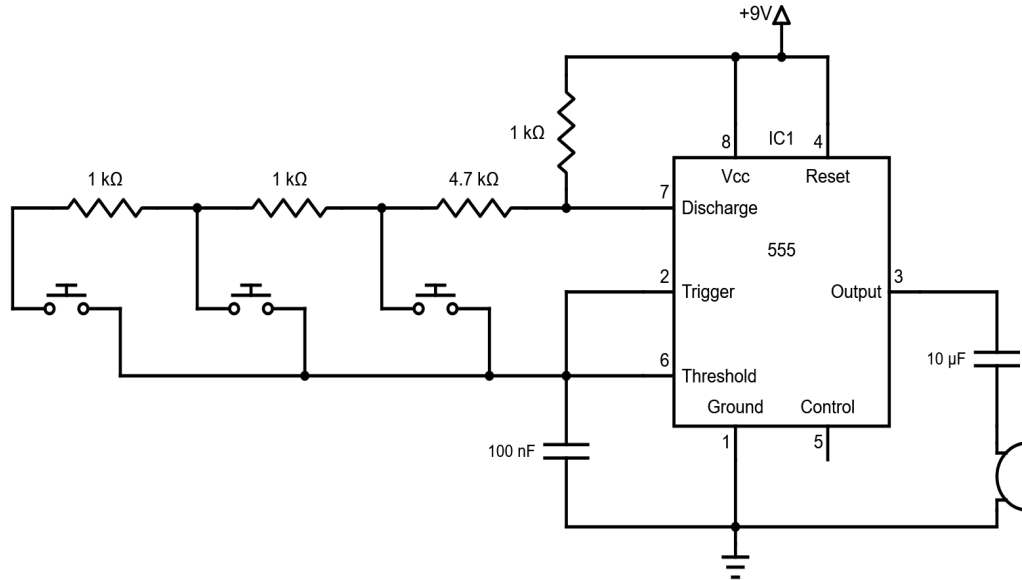
Exercise: How many nodes are in Project 2 (if the buttons are pressed)?



Node Exercise


Exercise: How many nodes are in Project 2 (if the buttons are not pressed)?

Answer: 9 Nodes

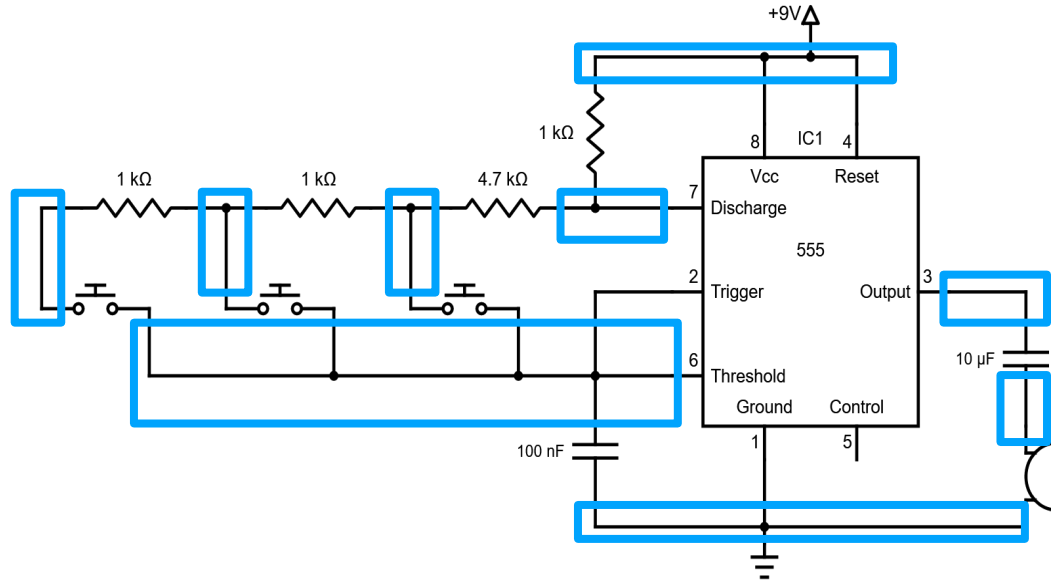



Nodes (Cont'd)

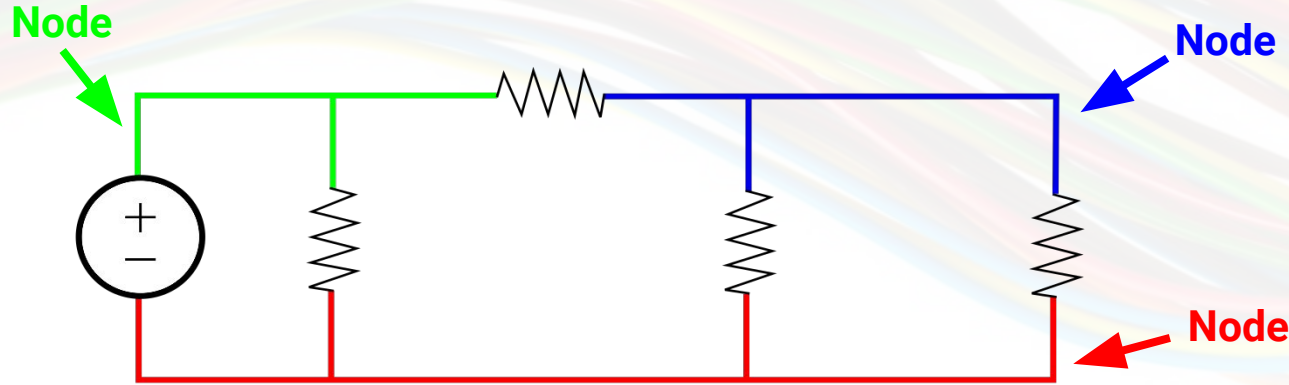- **Wires** can be treated as **nodes**
 - .. if we assume that the wire has **no resistance** and there is **no voltage change** across the wire
 - This is acceptable for our course projects




Nodes (Cont'd)

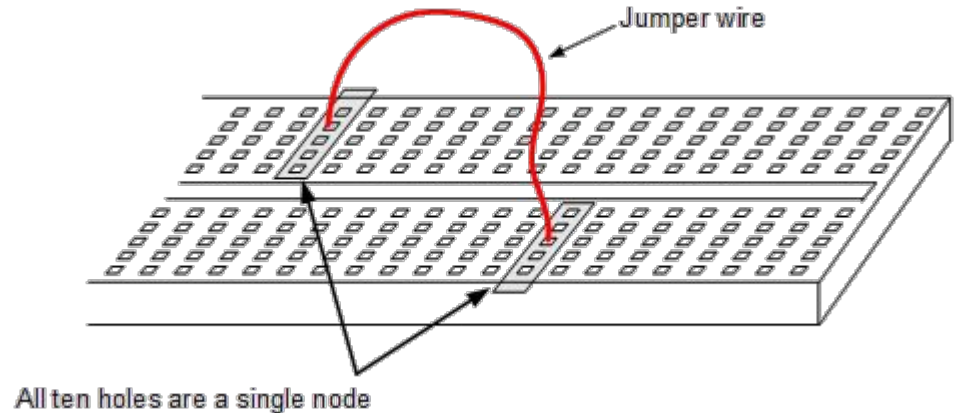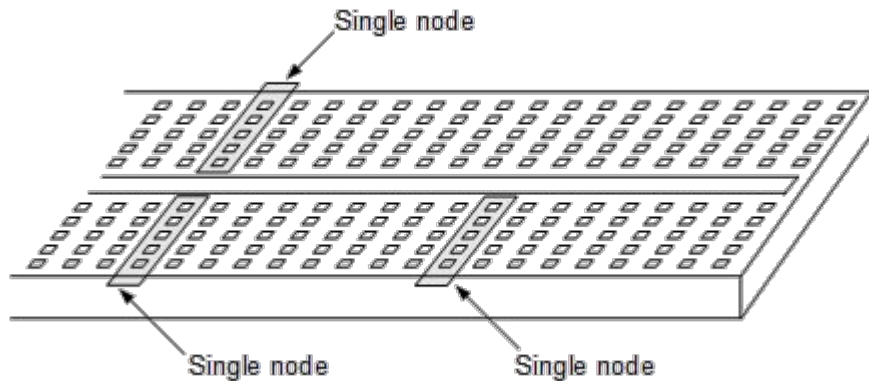- A breadboard horizontal **strip** be treated as a **single node**
- Connecting two strips with a jumper wire creates a larger **single node**
- Gap in the middle (called a **channel**) separates the left and right nodes on a breadboard



Nodes (Cont'd)

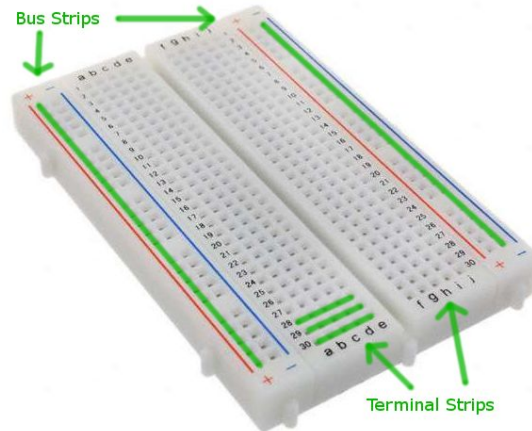
- A bus (vertical strip) on the breadboard is one long node
- Generally used for connecting a power source to the breadboard
 - (ex. Battery, power supply, etc.)
- Connect the positive terminal to the **power strip** (denoted by the + sign), and the negative terminal to the **ground strip** (denoted by the - sign)



Nodes (Cont'd)

I/A

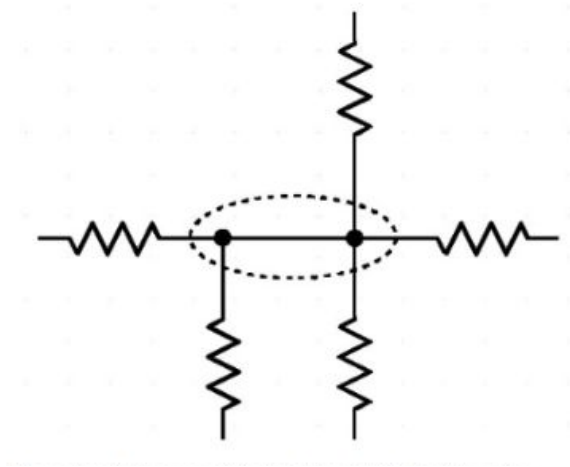What is the voltage difference between these two points?




Nodes (Cont'd)

What is the voltage difference between these two points?


Ex. $5V - 5V = 0V$

Answer: $0V$

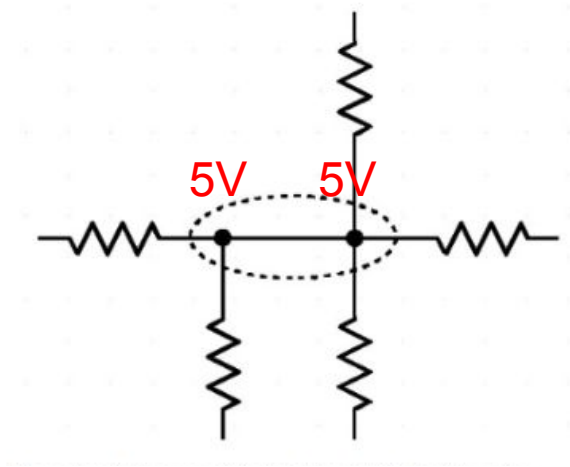


Voltage Drop

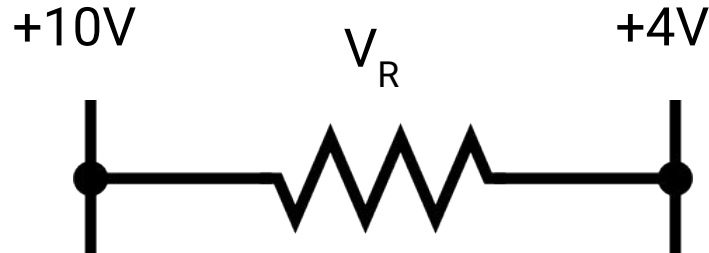- **Voltage drop** is the **difference of electric potential** (Volts) along the path of current flowing in a circuit
 - An LED experiences a voltage drop because it expends energy to emit light
- We can calculate the voltage drop between two nodes (across a circuit component)




Calculating Voltage Drop

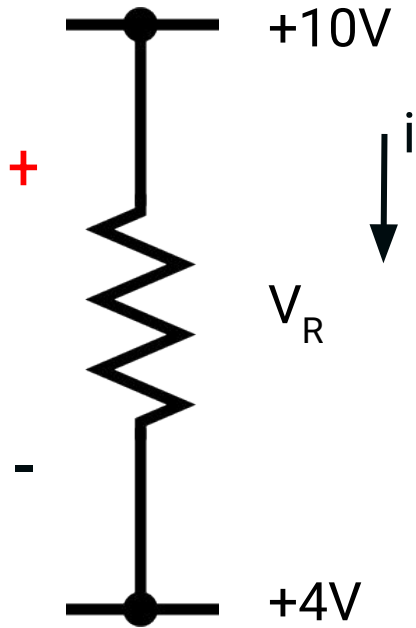

Find voltage drop V_R

1. Calculate V_R as the **difference in volts** between terminals, following the direction of current

Calculating Voltage Drop (Cont'd)

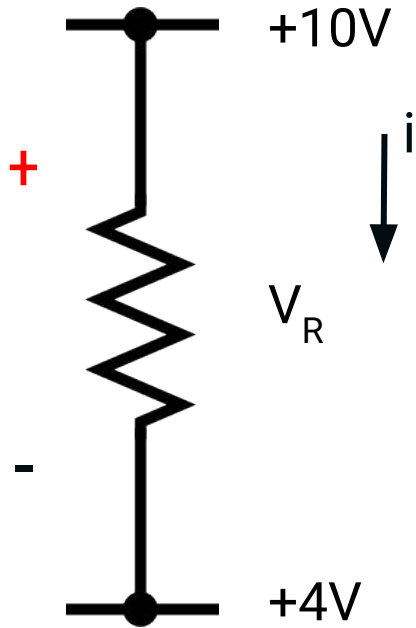


Find voltage drop V_R


1. Calculate V_R as the **difference in volts** between terminals, following the direction of current

$$V_R = 10V - 4V = 6V$$

Voltage Drop Sign Convention (Cont'd)

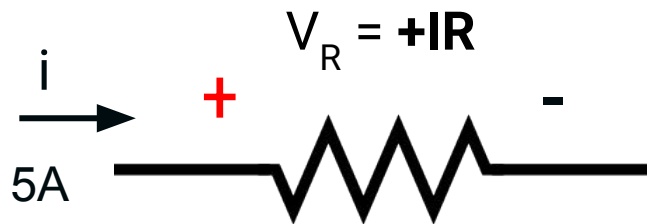


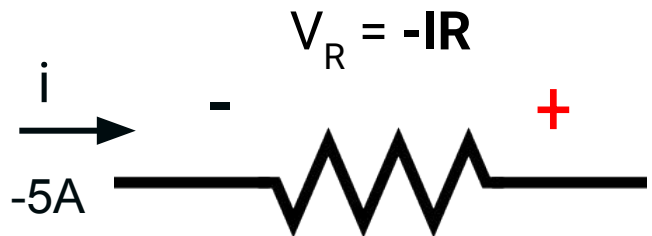
- The sign of the voltage drop is **positive** if current flows from $+$ to $-$ terminals
 - Conventional current flows from $+$ to $-$ terminals



- The sign of the voltage drop is **negative** if current flows $-$ to $+$ terminals

Voltage Drop for Project 2

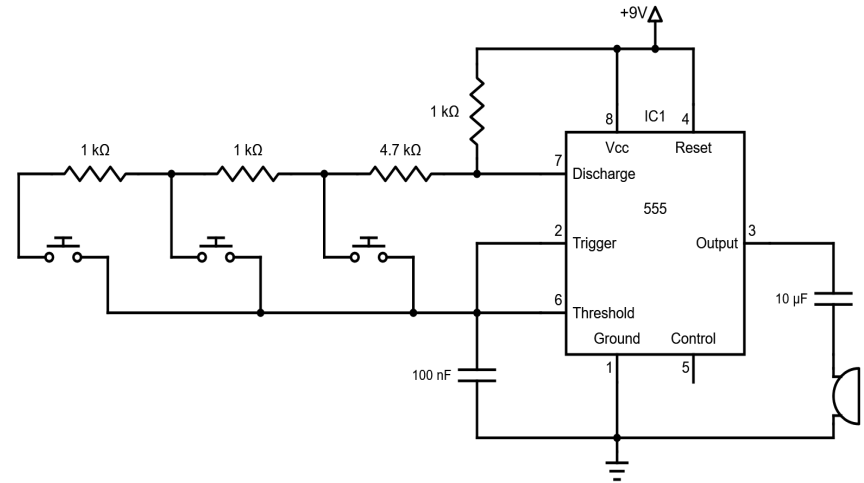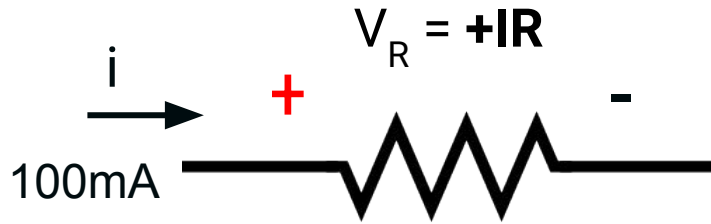
- By using different resistance values, we can vary the voltage drop across the resistors connected in series to produce 3 different sounds on the Piezo buzzer.



Series and Parallel Circuits


Series

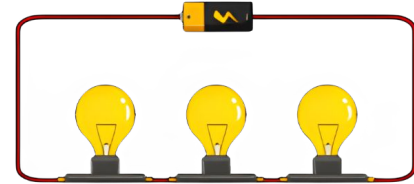- Two or more elements are in **series** if they exclusively are connected in one line
- Elements in series carry the **same current**



Parallel

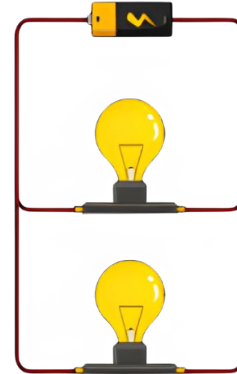- Two or more elements are in **parallel** if they are connected to they share the same two nodes
- Elements in parallel have the **same voltage** across them




Series and Parallel Circuits

- If **multiple resistors** are arranged **in series or parallel**, we can treat them as having a **single equivalent resistance**

Parallel
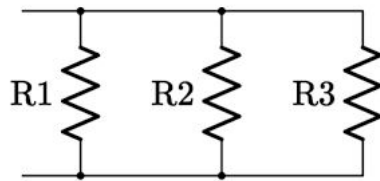
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



Series

$$R_{eq} = R_1 + R_2 + R_3$$



Resistors in Series

Ex) Given $R_1 = 10\Omega$, $R_2 = 30\Omega$, and $R_3 = 70\Omega$, we will find the equivalent resistance.




$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} = 10\Omega + 30\Omega + 70\Omega$$

$$R_{eq} = 110\Omega$$

Resistors in Parallel

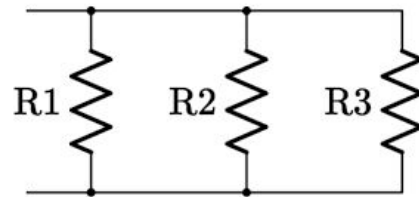Ex) Given $R_1 = 10\Omega$, $R_2 = 30\Omega$, and $R_3 = 70\Omega$, we will find the equivalent resistance.



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{10\Omega} + \frac{1}{30\Omega} + \frac{1}{70\Omega}$$

$$\frac{1}{R_{eq}} = \frac{31}{210}\Omega$$

$$R_{eq} = \frac{210}{31}\Omega$$

$$R_{eq} \simeq 6.77\Omega$$

SECTION IV

Multimeters

What is a Multimeter?

- A **multimeter** is an instrument used to measure the electrical properties of a circuit, including...
 - Voltage
 - Current
 - Resistance
 - Continuity
 - And More!



Multimeter Probes

- The multimeter has **two probes**:
 - The **red probe** is associated with the positive side of a component/connection
 - Plug it into the **red V** multimeter port
 - The **black probe** is associated with **COM**
 - Plug it into the **COM** multimeter port
 - **COM** or **common** is the reference point from which the red probe measures voltage, current, etc.
 - **Common is not ground**



Measuring Voltage

How to **measure DC voltage** with an auto-ranging multimeter:

- 1) Connect the probes to **VΩmA** and **COM**
- 2) Set the dial to **DC Voltage**
- 3) Place the **red probe** on one node and the **black probe** on the node to be used as the reference point
- 4) Read the display
 - The display value is the voltage drop from the node at the **red probe** to the node at the **black probe**



Measuring Resistance

How to **measure resistance** with an auto-ranging multimeter:

- 1) Connect the probes to **V Ω mA** and **COM**
- 2) Set the dial to **Ohms**
- 3) **Disconnect the component** from the live circuit
- 4) Place a probe on each terminal of the component
- 5) Read the display



Measuring Current

How to **measure DC current** with an auto-ranging multimeter:

- 1) Connect the probes to **A** and **COM**
- 2) Set the dial to **DC Current**
- 3) Place the probes in **series** with components in the circuit
- 4) Read the display



Testing Continuity

How to **test continuity** with an auto-ranging multimeter:


- 1) Connect the probes to **V Ω mA** and **COM**
- 2) Set the dial to **Continuity**
- 3) **Disconnect the power source** from the circuit
- 4) Place the probes on the circuit
- 5) The DMM **beeps** if there is a continuous path between the probes



Testing Continuity (Cont'd)

I/A

You can test the continuity across any two points on a circuit which lie on the same node. The DMM should beep

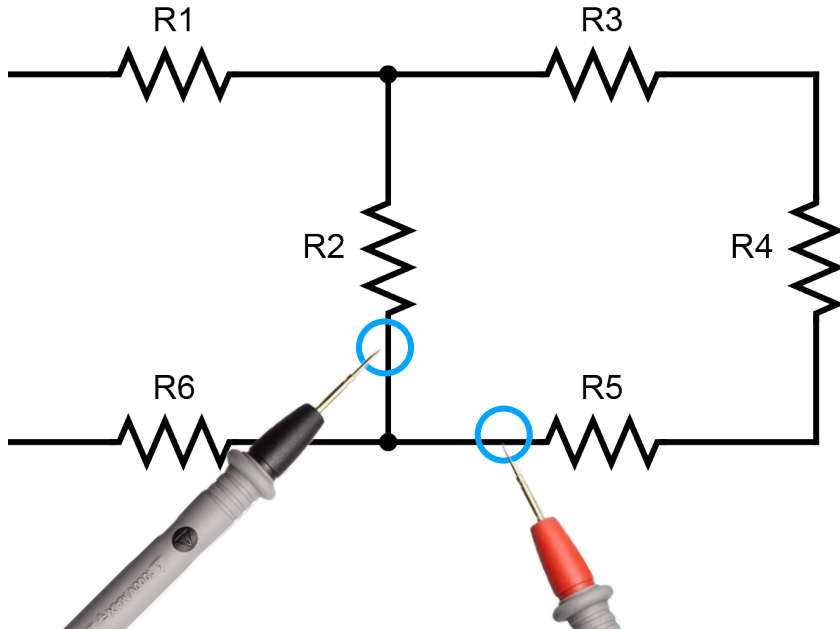

SECTION V

Troubleshooting Circuits

How To Troubleshoot a Circuit

Circuit not working? Follow these steps to **find the issue**:

1) Check the **power supply** and **ground**

- Is the power supply is providing the correct voltage?
 - Use a DMM to **measure voltage**
- Check the power and ground connections to the circuit

2) Visually **inspect the circuit**

- Look for loose connections, damaged components, cold solder joints, etc.
 - Use a DMM for **continuity tests**

How To Troubleshoot a Circuit (Cont'd)

Circuit not working? Follow these steps to **find the issue**:

3) Verify the **schematic diagram**

- Make sure you understand the circuit's functionality based on the schematic
- The circuit should match the **schematic diagram**. Go node-by-node and make sure every component is properly connected
- Check the component values against the schematic

How To Troubleshoot a Circuit (Cont'd)

Ideally, at this point, you have found the *potential issue*.

Here's how you verify the issue:

- Suspect a faulty component?
 - 1) **Replace the component** and test the circuit again
 - 2) Circuit still not functioning? Test the “faulty” component on a working circuit
 - If the “faulty” component works on another circuit, then go back to the start. Try to identify a new issue.
 - If it doesn't work, then use the replacement component. However, there's still work to be done: Your circuit still functions, so there must be another issue.

How To Troubleshoot a Circuit (Cont'd)

Ideally, at this point, you have found the *potential issue*.

Here's how you verify the issue:



- Loose wire? Poor connection?
 - 1) Re-solder or replace connections as needed and test the circuit again
 - 2) If the circuit still fails, **test the connections again** with the multimeter. It's possible to solder poorly on even the second or third try.

SECTION VI

Integrated Circuits


Integrated Circuits

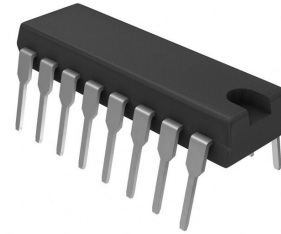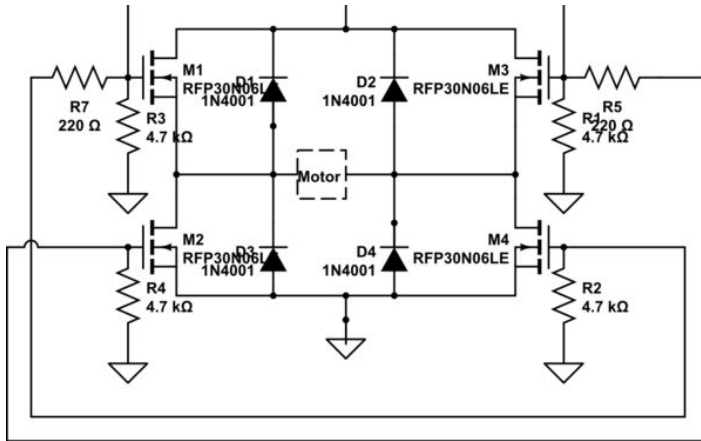- An **integrated circuit (IC, chip, microchip)** is a set of electronic circuits on one small flat piece of semiconductor material
 - Electronic components are **integrated** on the chip
 - Complex circuits can be **scaled down** and **mass-produced**



Integrated Circuits

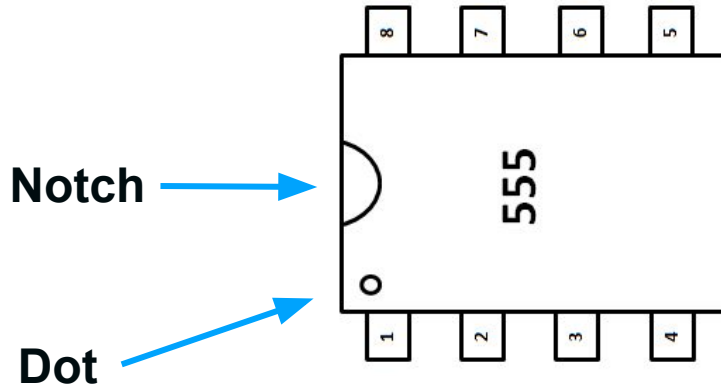- The **functions** and **pin layout** of an IC are specified in its **datasheet**
- The **notch/dot** on the IC indicates its **orientation**



www.ti.com

NA555, NE555, SA555, SE555

SLFS022I – SEPTEMBER 1973 – REVISED SEPTEMBER 2014

6 Pin Configuration and Functions

Pin Functions


NAME	PIN		I/O	DESCRIPTION
	D, P, PS, PW, JG	FK NO.		
CONT	5	12	I/O	Controls comparator thresholds. Outputs 2/3 VCC, allows bypass capacitor connection
DISCH	7	17	O	Open collector output to discharge timing capacitor
GND	1	2	–	Ground
NC		1, 3, 4, 6, 8, 9, 11, 13, 14, 16, 18, 19	–	No internal connection
OUT	3	7	O	High current timer output signal
RESET	4	10	I	Active low reset input forces output and discharge low.
THRES	6	15	I	End of timing input. THRES > CONT sets output low and discharge low
TRIG	2	5	I	Start of timing input. TRIG < 1/2 CONT sets output high and discharge open
V _{CC}	8	20	–	Input supply voltage, 4.5 V to 16 V. (SE555 maximum is 18 V)

SECTION VII


555 Timer IC

555 Timer IC

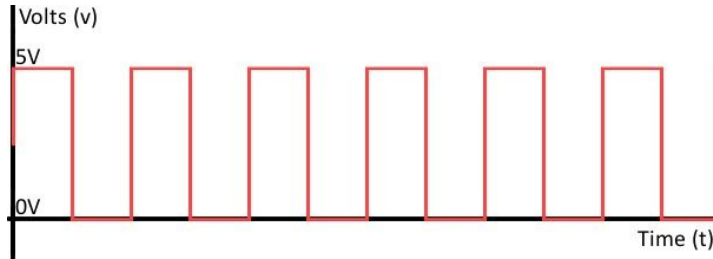
- The **555 Timer** is a chip used in various modes as a timer, pulse generator, wave oscillator, and an analog-to-digital signal converter
- In this course, the 555 Timer will be used in **astable mode** to generate an **oscillating digital wave**



Oscillating Digital Waveform

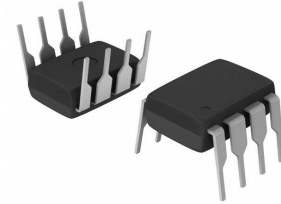


555 Timer DIP Package

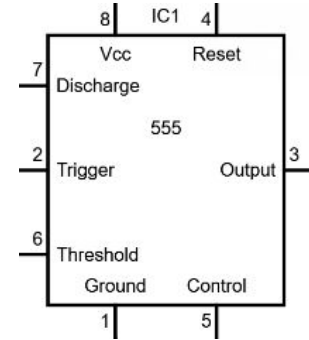

555 Timer Schematic Symbol

Blinking LED Circuit

- To further examine the astable-mode behavior of the 555 Timer, we will use it in a **blinking LED circuit** as an example
- The function of the the circuit is to **cycle an LED ON** and OFF at a constant frequency
- The circuit's timing relies on a the value of the **capacitor**

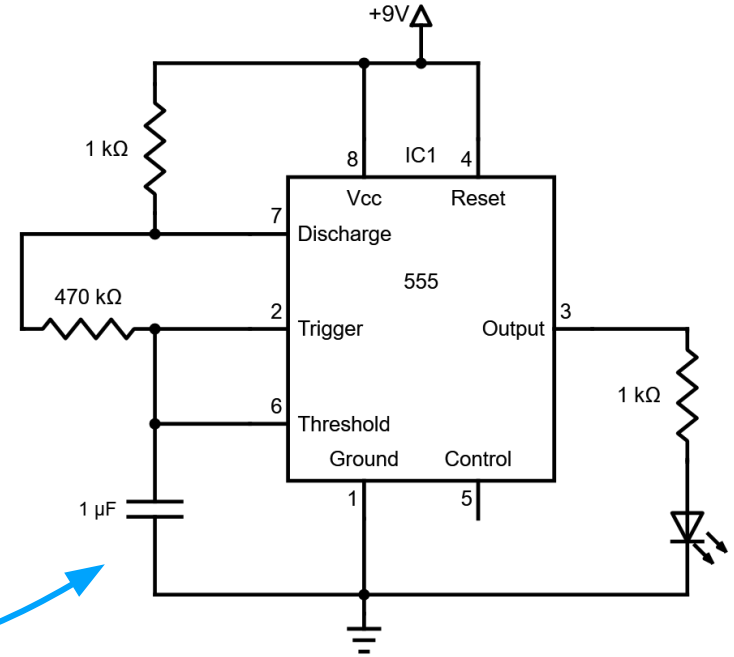


SECTION VIII

Other Project 2 Components

Capacitors

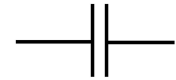
- A **capacitor** stores electrical energy which it charges and discharges
 - The ability of a capacitor to store energy is its **capacitance**, measured in **Farads (F)**
- Unlike a battery, a capacitor can only briefly store a small amount of energy
- When a capacitor is connected to a voltage source, it charges until it reaches the **same voltage** as the voltage source



Capacitor Timing Diagram


Timing Diagram

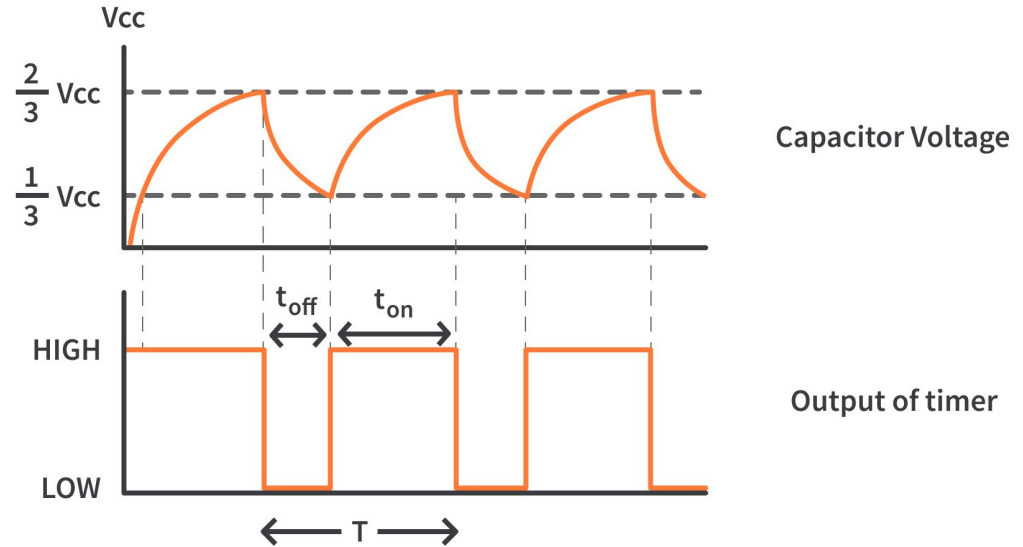- As the capacitor charges...
 - Output = **HIGH** voltage
- As the capacitor discharges...
 - Output = **LOW** voltage
- The output waveform is a **rectangular wave**





Piezo Buzzers

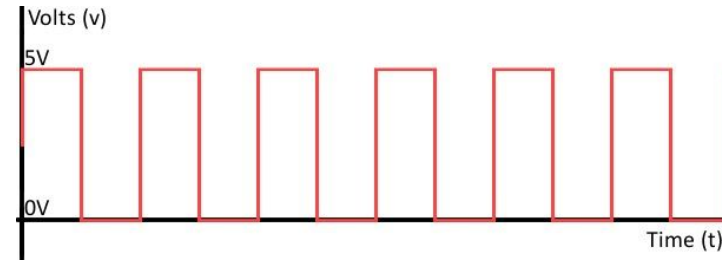- A piezoelectric buzzer is a component used to emit sound
- We will be using Passive Piezo Buzzers
 - They have to be fed an oscillating signal
 - Make sure to have the correct polarity




Printed Circuit Board (PCB)

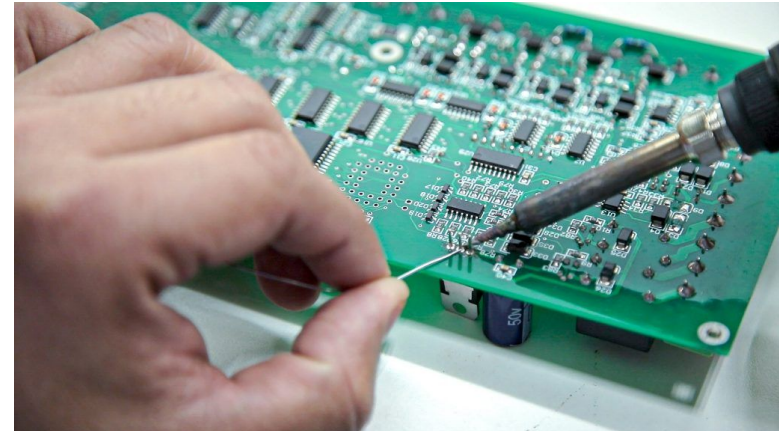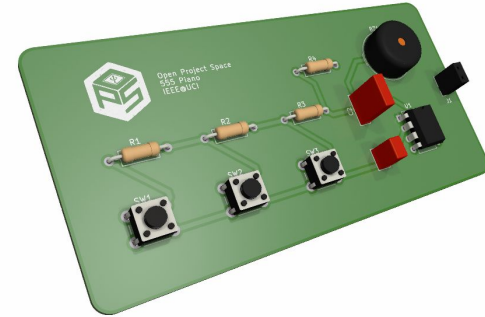- Breadboards and protoboards are great for prototyping simple circuits
- When electronics are more complex or are ready for production, we typically use printed circuit boards or PCBs.
- We will be using Passive Piezo Buzzers
 - They have to be fed an oscillating signal
 - Make sure to have the correct polarity



Sign-Up for the Workshop

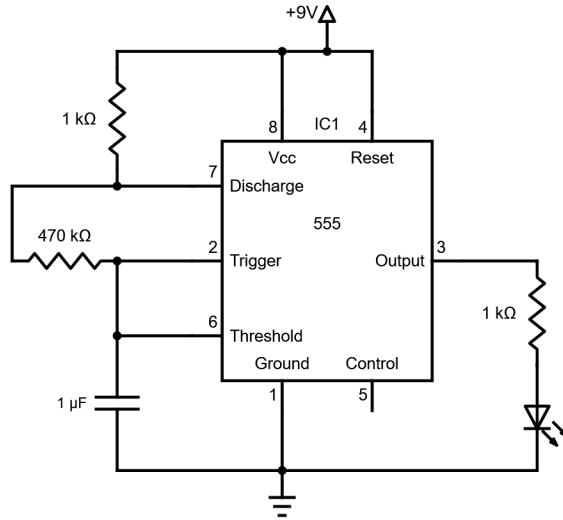- Thank you for attending the second lecture!
- The remainder of time will be to work on Project 2, Checkpoint 1: Blinking LED Circuit
- To solder your Project 2 PCBs, RSVP for a soldering workshop here:



FAIR USE DISCLAIMER

Copyright Disclaimer under section 107 of the Copyright Act 1976, allowance is made for “fair use” for purposes such as criticism, comment, news reporting, teaching, scholarship, education and research.

Fair use is a use permitted by copyright statute that might otherwise be infringing.

Non-profit, educational or personal use tips the balance in favor of fair use.